
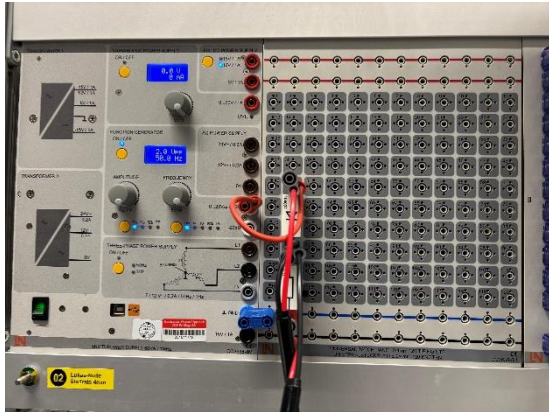


## Task-1:

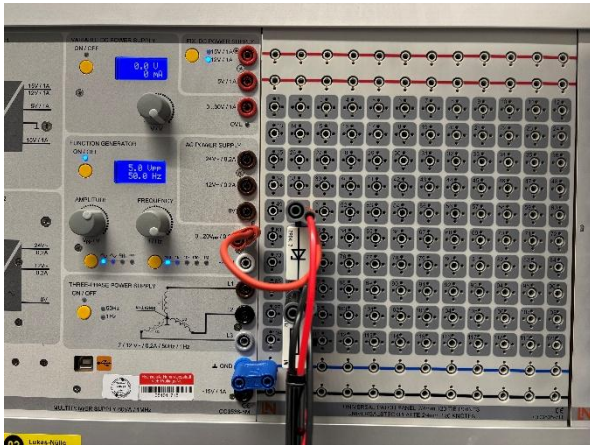


Applying  $V_{ss} = i_D \cdot R + V_D$  on the result and it matched.

## Task-2:



Here , we see that reverse current  $i_D = 0$ , and breakdown voltage  $V_D = 4.7$  V


## Task-3:

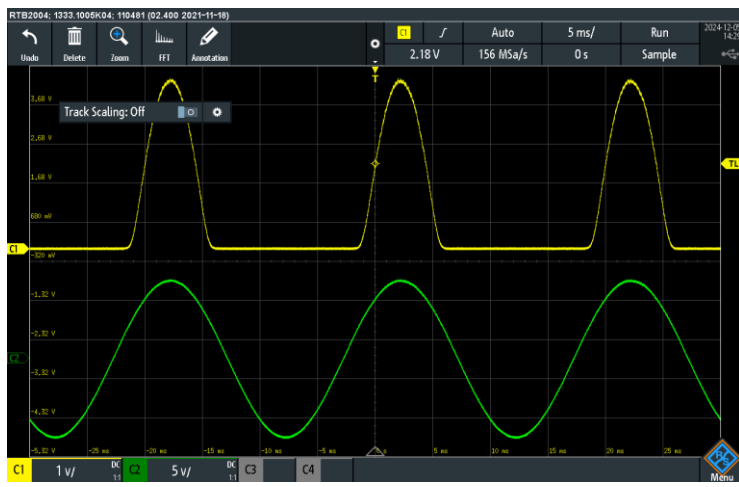

We got;

$$V_R = V_S - (V_{D1} + V_{D2}) = 4.7V$$

### Task-4:

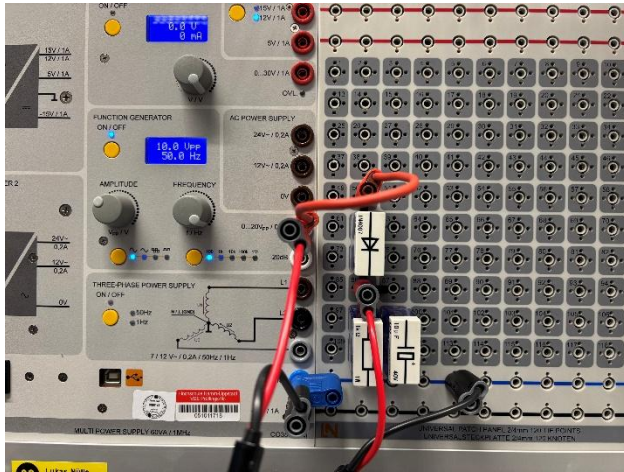

Output Voltage (Rectified Peak): 4.35V

**Ripple Voltage ( $V_{\text{ripple}}$ ) =  $V_{\text{out(max)}}$  –  $V_{\text{in(min)}}$  = 4.35-0.940=3.4V**